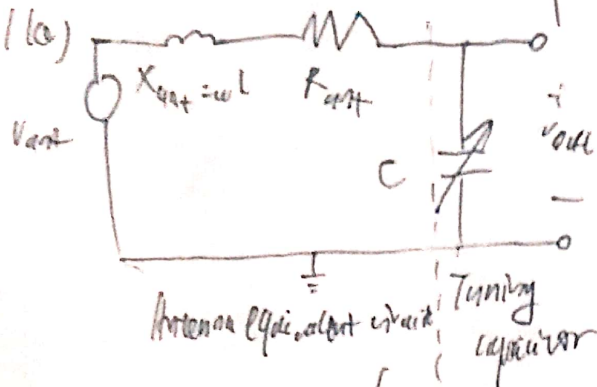


UE 216 Pre lab 2 Circuits 2/28/11 5:80 PM 1/10/2011

3.1(a)



$$\frac{V_{out}}{\frac{1}{j\omega C}} = \frac{V_{ant}}{j\omega L + R + \frac{1}{j\omega C}}$$

The frequency response function

$$H(j\omega) = \frac{V_{out}(j\omega)}{V_{ant}(j\omega)} = \frac{\frac{1}{j\omega C}}{j\omega L + R + \frac{1}{j\omega C}} = \frac{1}{- \omega^2 LC + j\omega RC + 1}$$

$$s = j\omega$$

$$H(s) = \frac{1}{LCs^2 + RCs + 1}$$

(b) Eq. (12.2.4) $f = \frac{1}{2\pi} \frac{1}{\sqrt{LC}} \text{ Hz}$ or $\omega_{res} = \frac{1}{\sqrt{LC}} \text{ rad/s}$

Eq. (12.2.6) $BW_{dB} = \frac{1}{2\pi} \frac{R}{L} \text{ Hz}$

Eq. (12.2.7) $Q = 2\pi f_{res} \frac{L}{R} = \frac{1}{\sqrt{LC}} \frac{L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{f}{BW_{dB}}$

Values read off from the plot:


	Peak Freq (kHz)	3dB BW (kHz)	Quality Factor
C = 100pF	513.65	3.312	155.09
C = 30pF	937.17	14.685	63.86

Values computed from the equations

	Peak Freq (kHz)	3dB BW (kHz)	Quality Factor
C = 100pF	513.67	3.316	154.92
C = 30pF	937.83	14.921	62.85

Plot see attached pages

3.2 (a)

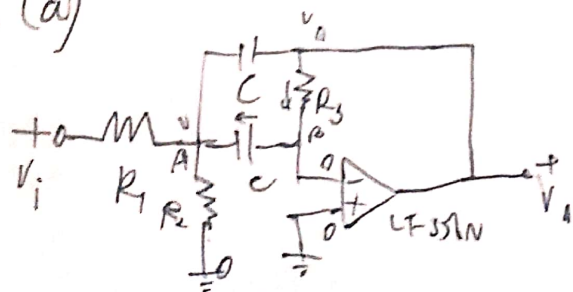

At node 1

$$\frac{V_i - V}{R_1} + \frac{V_o - V}{\frac{1}{j\omega C}} + \frac{V_o}{R_3} = \frac{V}{R_2}$$

$$V_o - V = \frac{V_o}{R_3} (R_3 + \frac{1}{j\omega C}) = V_o + \frac{V_o}{j\omega R_3 C}$$

$$\frac{V_i}{R_1} + \frac{V_o}{j\omega R_1 R_3 C} + j\omega C V_o + \frac{2V_o}{R_3} = -\frac{V_o}{j\omega R_2 R_3 C}$$

$$\frac{V_i}{R_1} = -V_o \left(\frac{1}{j\omega R_1 R_3 C} + \frac{2}{R_3} + j\omega C + \frac{1}{j\omega R_2 R_3 C} \right)$$

$$H_x(j\omega) = \frac{V_o}{V_i} = \frac{1}{\left(\frac{1}{j\omega R_1 R_3 C} + \frac{2}{R_3} + j\omega C + \frac{1}{j\omega R_2 R_3 C} \right)}$$

$$= \frac{1}{\frac{R_1}{j\omega R_2 R_3 C} + \frac{2R_1}{R_3} + j\omega R_1 C + \frac{1}{j\omega R_3 C}} = \frac{-j\omega R_1 R_3 C}{R_1 + 2j\omega R_1 R_3 C - \omega^2 R_1 R_2 R_3 C^2 + R_3}$$

$$= \frac{-j\omega R_2 R_3 C / (R_1 + R_3)}{-\omega^2 \frac{R_1 R_2 R_3 C^2}{R_1 + R_3} + j\omega \frac{R_1 R_3 C}{R_1 + R_3} + 1} = \frac{-R_2 R_3 C / (R_1 + R_3) s}{\frac{R_1 R_2 R_3 C^2}{R_1 + R_3} s^2 + \frac{2R_1 R_3 C}{R_1 + R_3} s + 1}$$

$$\left[\begin{aligned} a_2 &= \frac{R_1 R_2 R_3 C^2}{R_1 + R_3} & a_3 &= \frac{2R_1 R_3 C}{R_1 + R_3} & H_{1x}(j\omega) &= \frac{-\frac{R_2 R_3 C}{R_1 + R_3} s}{\frac{R_1 R_2 R_3 C^2}{R_1 + R_3} s^2 + \frac{2R_1 R_3 C}{R_1 + R_3} s + 1} \end{aligned} \right]$$

$R_1 = 10^3 \Omega$ $R_2 = 10^4 \Omega$ $R_3 = 10^2 \Omega$ $C = 1.5 \times 10^{-8} F$

$$\begin{aligned} a_1 &= -1.607 \times 10^{-6} \\ a_2 &= 2.411 \times 10^{-13} \\ a_3 &= 3.214 \times 10^{-6} \end{aligned}$$

(b) $H(s) = H_0 \frac{\beta s}{s^2 + \beta s + \omega_0^2}$ $H(j\omega) = H_0 \frac{1}{\frac{\omega}{\omega_0} + j \frac{(\omega/\omega_0)^2 - 1}{\beta/\omega_0}}$ $\approx H_0 \frac{1}{1 + j \frac{\omega}{\omega_0} \frac{\beta}{\omega_0}}$ $\beta/\omega_0 \approx \beta$ when $\beta \ll \omega_0$

Formulas:

The peak value of the frequency response function H_0 , the 3-dB bandwidth β

$$H_{1x}(s) = \frac{-\frac{1}{R_3 C} s}{s^2 + \frac{2}{R_3 C} s + \frac{R_1 + R_2}{R_1 R_2 R_3 C^2}} = -\frac{R_3}{2R_1} \frac{\frac{2}{R_3 C} s}{s^2 + \frac{2}{R_3 C} s + \frac{R_1 + R_2}{R_1 R_2 R_3 C^2}}$$

$$\left[\begin{aligned} H_0 &= -\frac{R_3}{2R_1} & \beta &= \frac{2}{R_3 C} & \omega_0 &= \sqrt{\frac{R_1 + R_2}{R_1 R_2 R_3 C^2}} \end{aligned} \right]$$

The center of the passband in frequency

$$f = \frac{\omega_0}{2\pi} = \frac{1}{2\pi} \sqrt{\frac{R_1 + R_2}{R_1 R_2 R_3 C^2}}$$

using eq. (2.5.2) through (2.5.5)
that $\beta \ll \omega_0$ so we can use $\beta/\omega_0 \approx \beta$

eq. (2.5.4) shows $H(j\omega)$ achieves a maximum value of H_0 at ω_0 , i.e. the peak value of the frequency response function

Numerical values: Substituting given values in formulas above

$\boxed{H_0 = -5}$ $\boxed{\beta = 1.33 \times 10^5 \text{ Hz}}$ $\boxed{f = 1.025 \times 10^5 \text{ Hz}}$
 peak value of $H(f_{IF})$ 3dB bandwidth of IF center of the passband

(c) The graph see attached pages

3.3 a) Carrier frequency $f_c = 1600 \text{ kHz}$

IF filter centered at $f_{IF} = 100 \text{ kHz}$ $f_c > f_{IF}$

LO frequency $f_{L0} = f_c - f_{IF} = 1500 \text{ kHz}$

$f_{L0} = f_c + f_{IF} = 1700 \text{ kHz}$

For $f_{L0} = 1500 \text{ kHz}$ the frequency band centered at f_{img} known as image band

$f_{\text{img}} = f_c + 2f_{IF} = 1800 \text{ kHz}$

For $f_{L0} = 1700 \text{ kHz}$,

$f_{\text{img}} = |f_{IF} - f_{L0}| = |2f_{IF} - f_c| = 1400 \text{ kHz}$

b) $f_c = 530 \text{ kHz}$ $f_{IF} = 100 \text{ kHz}$

LO frequency $f_{L0} = f_c - f_{IF} = 430 \text{ kHz}$, image band center $f_{\text{img}} = |2f_{IF} - f_c| = 330 \text{ kHz}$


$f_{L0} = f_c + f_{IF} = 630 \text{ kHz}$, image band center $f_{\text{img}} = f_c + 2f_{IF} = 730 \text{ kHz}$

$f_c (\text{kHz})$	$f_{L0} (\text{kHz})$	$f_{L02} (\text{kHz})$	$f_{\text{image1}} (\text{kHz})$	$f_{\text{image2}} (\text{kHz})$
1600	1500	1700	1800	1400
530	430	630	330	730

3. ψ Equivalency of Figs 2.4.2

that $\frac{1}{2}f_{IF} < f_c < f_{IF}$

$$f_{LO} = f_c - f_{IF}$$

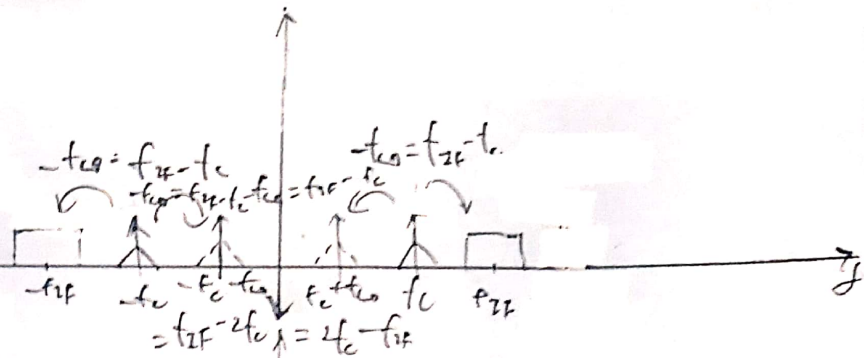

Equivalency of Figs 2.4.3

that $\frac{1}{2}f_{IF} < f_c < f_{IF}$

$$f_{LO} = f_c + f_{IF}$$

